



ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 21

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

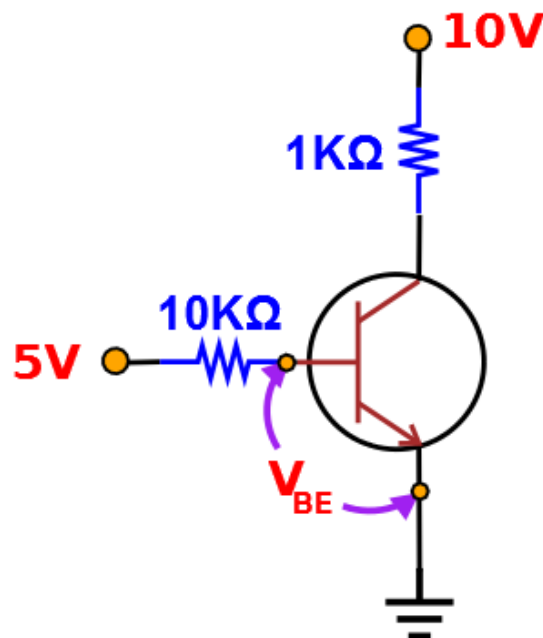Question 21: What is the value of V_{BE} voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 22

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

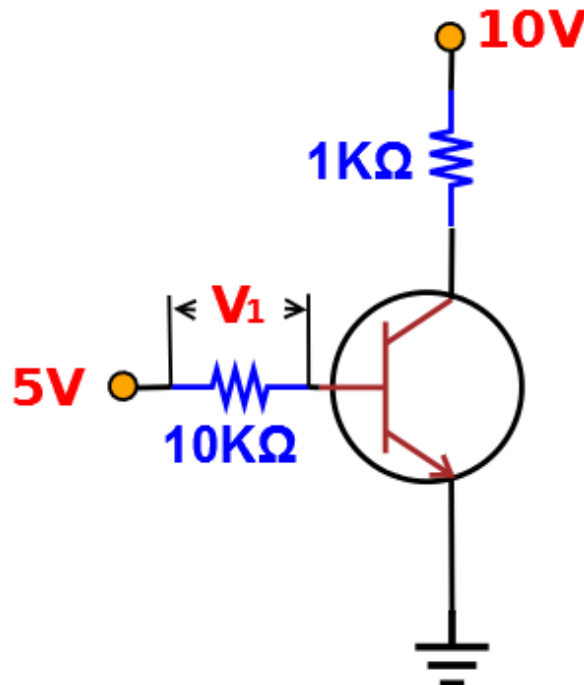
Question 22: What is the value of V_1 Voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 23

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

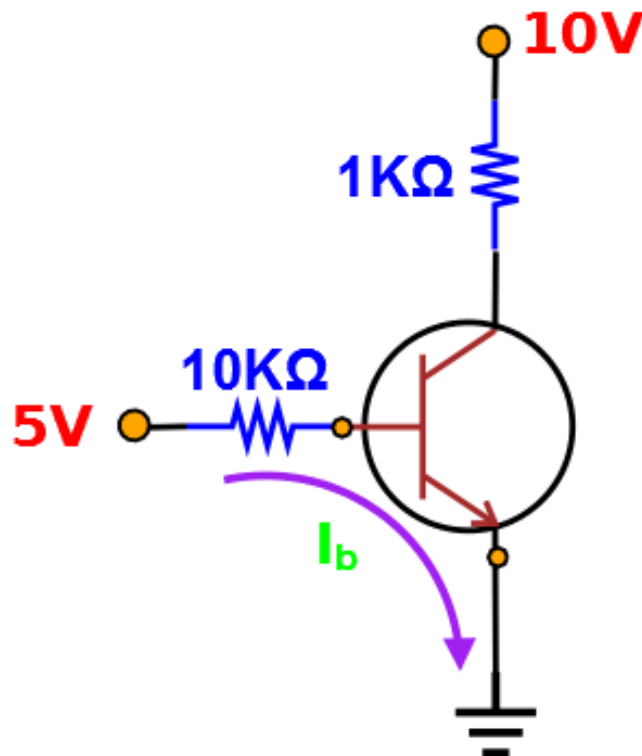
Question 23: What is the value of I_b Current?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 24

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

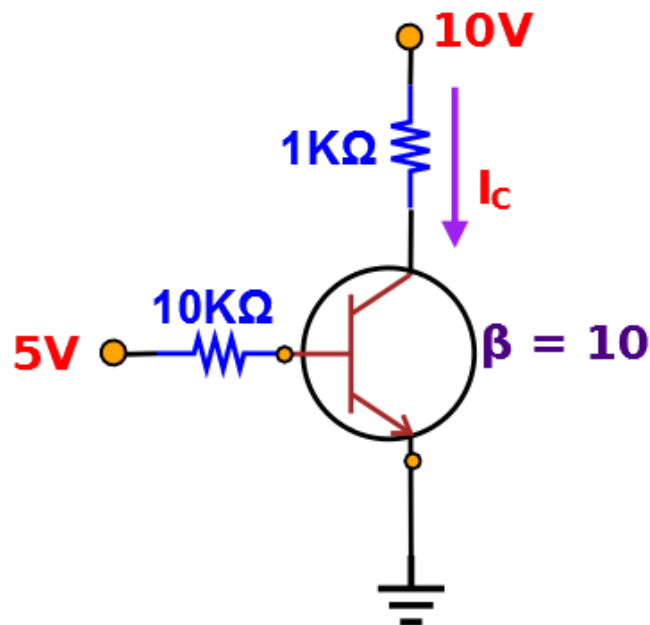Question 24: What is the value of I_c Current?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 25

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

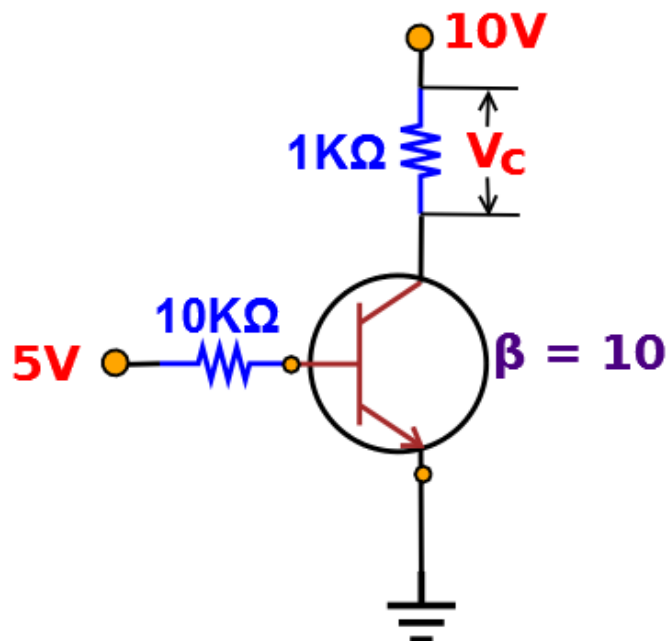Question 55: What is the value of V_c Voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 26

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

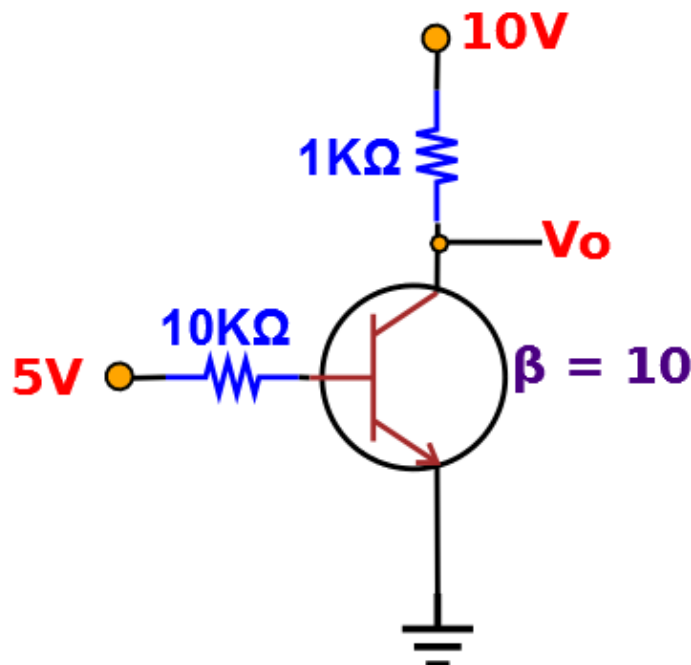Question 26: What is the value of V_o voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 27

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

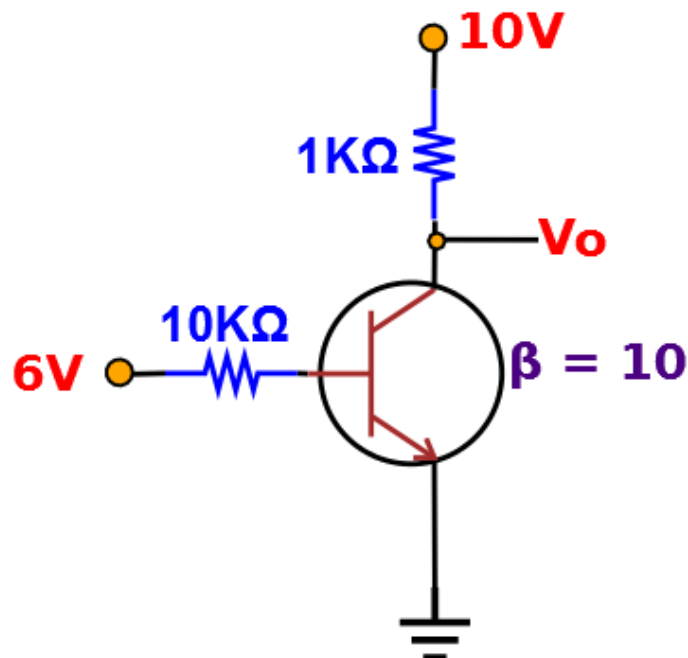Question 27: What is the value of V_o voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 28

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

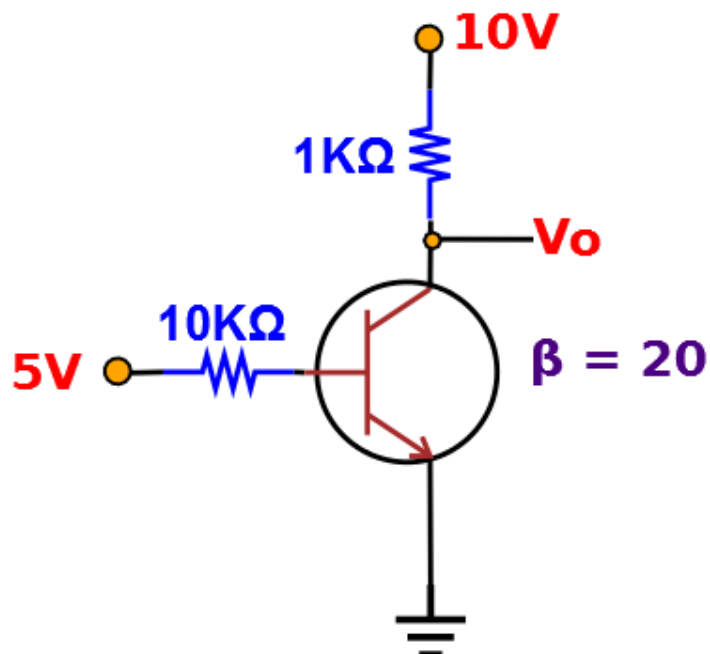Question 28: What is the value of V_o voltage?





ECEN Academy

www.ecenacademy.com


 - (91) 97908 73099

Analog Electronics Problem – 29

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

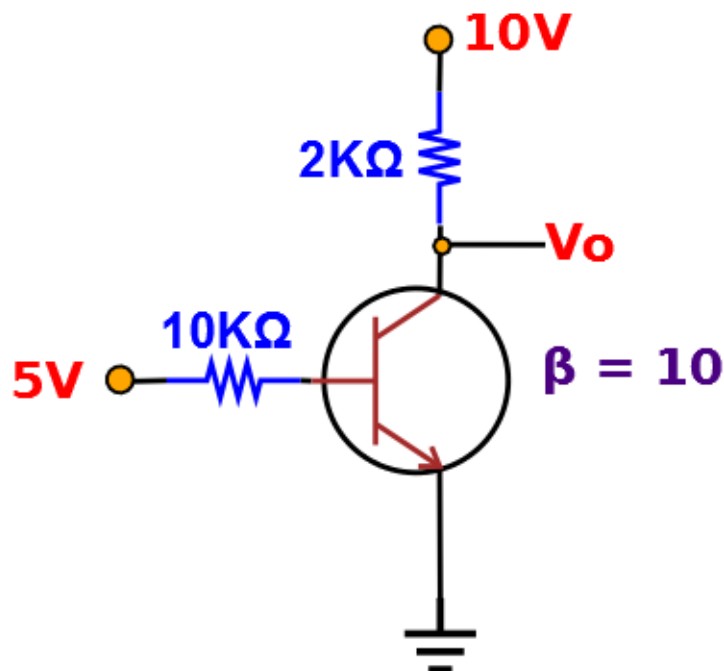Question 29: What is the value of V_o voltage?





ECEN Academy

www.ecenacademy.com

 - (91) 97908 73099

Analog Electronics Problem – 30

Instructions:

1. Do not discuss with any one while solving the problems
2. Do not use internet while solving the problems
3. Do not use books while solving the problems
4. Do not try to copy from others
5. Do the problems in an easy way.

Question 30: What is the value of V_o voltage?

